

x7segl.vhd : Afficheur 7 segments

```
entity x7seg is
  Port ( sw : in STD_LOGIC_VECTOR (3 downto 0);
        sevenseg : out STD_LOGIC_VECTOR (6 downto 0));
end x7seg;
```

architecture Behavioral of x7seg is

begin

with sw select

```
  sevenseg <= "1000000" when "0000",
    "1111001" when "0001",
    "0100100" when "0010",
    "0110000" when "0011",
    "0011001" when "0100",
    "0010010" when "0101",
    "0000010" when "0110",
    "1111000" when "0111",
    "0000000" when "1000",
    "0010000" when "1001",
    "0001000" when "1010",
    "0000011" when "1011",
    "1000110" when "1100",
    "0100001" when "1101",
    "0000110" when "1110",
    "0001110" when others;
```

end Behavioral;

toplevel.vhd : Afficher sur les leds, la valeur inverse des switch bit à bit

entity toplevel is

```
  Port ( sw : in STD_LOGIC_VECTOR (15 downto 0);
        led : out STD_LOGIC_VECTOR (15 downto 0));
```

end toplevel;

architecture Behavioral of toplevel is

begin

```
  led <= not sw;
```

end Behavioral;

my_add.vhd : Additionneur 4 bits

Un mot de 4 bits est saisi sur les 4 switches de droite, le second sur les 4 de gauche, l'affichage du résultat se fera sur les 5 leds de droites (retenue comprise)

entity my_add is

```
  Port ( sw : in STD_LOGIC_VECTOR (15 downto 0);
        led : out STD_LOGIC_VECTOR (4 downto 0));
```

end my_add;

architecture Behavioral of my_add is

begin

```
  led <= ('0' & sw(3 downto 0)) + ('0' & sw(15 downto 12));
```

end Behavioral;

x7seg.vhd (que pour ce TP!!!!)

```
entity x7seg is
  Port ( sw : in STD_LOGIC_VECTOR (3 downto 0);
        p : in STD_LOGIC_VECTOR (1 downto 0);
        sevenseg : out STD_LOGIC_VECTOR (6 downto 0));
end x7seg;
```

architecture Behavioral of x7seg is

```
begin
  PROCESS(sw, p)
  BEGIN
    IF (p = "00") THEN
      CASE sw IS
        when "0000" => sevenseg <= "1000000" ;
        when "0001" => sevenseg <= "1111001" ;
        when "0010" => sevenseg <= "0100100" ;
        when "0011" => sevenseg <= "0110000" ;
        when "0100" => sevenseg <= "0011001" ;
        when "0101" => sevenseg <= "0010010" ;
        when "0110" => sevenseg <= "0000010" ;
        when "0111" => sevenseg <= "1111000" ;
        when "1000" => sevenseg <= "0000000" ;
        when "1001" => sevenseg <= "0010000" ;
        when "1010" => sevenseg <= "0001000" ;
        when "1011" => sevenseg <= "0000011" ;
        when "1100" => sevenseg <= "1000110" ;
        when "1101" => sevenseg <= "0100001" ;
        when "1110" => sevenseg <= "0000110" ;
        when "1111" => sevenseg <= "0001110" ;
        when others => sevenseg <= "0000000" ;
      END CASE;

      ELSIF (p = "01") THEN
        -- comparaison
        CASE sw IS
          when "0000" => sevenseg <= "0001110";
          when others => sevenseg <= "0000111";
        END CASE;

        ELSIF (p = "10") THEN
          -- parity
          CASE sw IS
            when "0000" => sevenseg <= "0001100";
            when others => sevenseg <= "1001111";
          END CASE;

          ELSE
            sevenseg <= "0000000";
          END IF;
        END PROCESS;
      end Behavioral;
```

comp.vhd

entity comp is

```
    Port ( a : in STD_LOGIC_VECTOR (7 downto 0);  
          b : in STD_LOGIC_VECTOR (7 downto 0);  
          res : out STD_LOGIC);
```

end comp;

architecture Behavioral of comp is

begin

```
    PROCESS(a,b)
```

```
    BEGIN
```

```
        IF a=b THEN res <= '1';
```

```
        ELSE res <= '0';
```

```
        END IF;
```

```
    END PROCESS;
```

end Behavioral;

count1.vhd

entity count1 is

```
    Port ( a : in STD_LOGIC_VECTOR (15 downto 0);  
          res : out STD_LOGIC_VECTOR (4 downto 0));
```

end count1;

architecture Behavioral of count1 is

begin

```
    PROCESS(a)
```

```
    VARIABLE nombre_1 : INTEGER;
```

```
    BEGIN
```

```
        nombre_1 := 0;
```

```
        FOR I IN 0 TO 15 LOOP
```

```
            IF a(I) = '1' THEN
```

```
                nombre_1 := nombre_1 + 1;
```

```
            END IF;
```

```
        END LOOP;
```

```
        res <= conv_std_logic_vector(nombre_1, 5);
```

```
    END PROCESS;
```

end Behavioral;

parity.vhd

entity parity is

```
Port ( a : in STD_LOGIC_VECTOR (15 downto 0);  
      res : out STD_LOGIC);
```

end parity;

architecture Behavioral of parity is

begin

```
PROCESS(a)
```

```
VARIABLE nombre_1: STD_LOGIC;
```

```
BEGIN
```

```
    nombre_1 := '0';
```

```
    FOR I IN 0 TO 15 LOOP
```

```
        nombre_1 := nombre_1 XOR a(I);
```

```
    END LOOP;
```

```
    res <= nombre_1;
```

```
END PROCESS;
```

end Behavioral;

calc.vhd : Calculatrice

BTN 4	BTN 3	BTN 2	BTN 1	BTN 0	Action
0	0	0	0	0	addition 4 bits
0	0	0	0	1	and 4 bits
0	0	0	1	0	or 4 bits
0	0	0	1	1	xor 4 bits
0	0	1	x	x	comparateur 4 bits
0	1	0	x	x	parité 8 bits
1	0	0	x	x	count1 8 bits

entity calc is

```
Port ( sw : in STD_LOGIC_VECTOR (15 downto 0);
```

```
      btnR : in STD_LOGIC;
```

```
      btnL : in STD_LOGIC;
```

```
      btnC : in STD_LOGIC;
```

```
      btnU : in STD_LOGIC;
```

```
      btnD : in STD_LOGIC;
```

```
      led : out STD_LOGIC_VECTOR (15 downto 0);
```

```
      seg : out STD_LOGIC_VECTOR (6 downto 0);
```

```
      an : out STD_LOGIC_VECTOR (3 downto 0));
```

end calc;

architecture Behavioral of calc is

component add4

```
Port ( a : in STD_LOGIC_VECTOR (3 downto 0);
```

```
      b : in STD_LOGIC_VECTOR (3 downto 0);
```

```
      sum : out STD_LOGIC_VECTOR (4 downto 0));
```

end component;

```

component x7seg
  Port ( sw : in STD_LOGIC_VECTOR (3 downto 0);
        p : in STD_LOGIC_VECTOR (1 downto 0);
        sevenseg : out STD_LOGIC_VECTOR (6 downto 0));
end component;

```

```

component comp
  Port ( a : in STD_LOGIC_VECTOR (7 downto 0);
        b : in STD_LOGIC_VECTOR (7 downto 0);
        res : out STD_LOGIC);
end component;

```

```

component parity
  Port ( a : in STD_LOGIC_VECTOR (15 downto 0);
        res : out STD_LOGIC);
end component;

```

```

component count1
  Port ( a : in STD_LOGIC_VECTOR (15 downto 0);
        res : out STD_LOGIC_VECTOR (4 downto 0));
end component;

```

```

signal sig : std_logic_vector (4 downto 0);
signal s_add, s_and, s_or, s_xor : std_logic_vector(4 downto 0);
signal s_comp, s_parity : std_logic;
signal s_count1 : STD_LOGIC_VECTOR (4 downto 0);
signal btn : std_logic_vector (4 downto 0);
signal combi : STD_LOGIC_VECTOR (7 downto 0);
signal aff : STD_LOGIC_VECTOR (1 downto 0);

```

```

begin

```

```

  cmp_add : add4 port map (a=>sw(15 downto 12), b=>sw(3 downto 0), sum=>s_add);
  s_and <= ('0' & sw(15 downto 12)) AND ('0' & sw(3 downto 0));
  s_or <= ('0' & sw(15 downto 12)) OR ('0' & sw(3 downto 0));
  s_xor <= ('0' & sw(15 downto 12)) XOR ('0' & sw(3 downto 0));
  cmp_comp : comp port map (a=>sw(15 downto 8), b=>sw(7 downto 0), res=>s_comp);
  cmp_parity : parity port map (a=>sw, res=>s_parity);
  cmp_count1 : count1 port map (a=>sw, res=>s_count1);

```

```

  btn <= btnU & btnC & btnD & btnL & btnR;

```

with btn select

```
sig <= s_add when "00000",
    s_and when "00001",
    s_or when "00010",
    s_xor when "00011",

    "0000" & s_comp when "00100",
    "0000" & s_comp when "00101",
    "0000" & s_comp when "00110",
    "0000" & s_comp when "00111",

    "0000" & s_parity when "01000",
    "0000" & s_parity when "01001",
    "0000" & s_parity when "01010",
    "0000" & s_parity when "01011",

    s_count1 when "10000",
    s_count1 when "10001",
    s_count1 when "10010",
    s_count1 when "10011",

    "00000" when others;
```

with btn select

```
aff <= "01" when "00100",
    "01" when "00101",
    "01" when "00110",
    "01" when "00111",

    "10" when "01000",
    "10" when "01001",
    "10" when "01010",
    "10" when "01011",

    "00" when "00000",
    "00" when "00001",
    "00" when "00010",
    "00" when "00011",

    "00" when "10000",
    "00" when "10001",
    "00" when "10010",
    "00" when "10011",

    "11" when others;
```

cmp_x7seg : x7seg port map (sw=>sig(3 downto 0), p=>aff, sevenseg=>seg);

led <= "000000000000" & sig;

an <= x"e";

end Behavioral;

fpd.vhd : Bascule D (utile pour mémoriser l'état précédent)

```
entity fpd is
  GENERIC (init_value: STD_Logic := '0');
  Port ( d : in  STD_LOGIC;
        q : out STD_LOGIC:= init_value;
        clk : in  STD_LOGIC);
end fpd;

architecture Behavioral of fpd is
begin
  process (clk)
  begin
    if (clk'event and clk='1') then
      q <= d;
    end if ;
  end process ;
end Behavioral;
```

shift.vhd : 1 fpd pour chaque led + relier les entrées et sorties - Bascule 0 démarre à 1 contrairement aux autres (0)

```
entity shift is
  Port ( btn : in STD_LOGIC_VECTOR (4 downto 0);
        sw : in STD_LOGIC_VECTOR (15 downto 0);
        led : out STD_LOGIC_VECTOR (15 downto 0);
        clk : in  STD_LOGIC);
end shift;

architecture Behavioral of shift is

  signal Q0, Q1, Q2, Q3, Q4, Q5, Q6, Q7, Q8, Q9, Q10, Q11, Q12, Q13, Q14, Q15 : std_logic;

  component fpd
    GENERIC (init_value: STD_Logic := '0');
    Port ( d, clk : in  STD_LOGIC;
          q : out STD_LOGIC:= init_value);
  end component;

begin
  d0: fpd GENERIC MAP(init_value => '1') PORT MAP(d => Q15,q => Q0, clk => clk);
  d1: fpd PORT MAP(d=> Q0, q=>Q1, clk=>clk);
  d2: fpd PORT MAP(d=> Q1, q=>Q2, clk=>clk);
  d3: fpd PORT MAP(d=> Q2, q=>Q3, clk=>clk);
  d4: fpd PORT MAP(d=> Q3, q=>Q4, clk=>clk);
  d5: fpd PORT MAP(d=> Q4, q=>Q5, clk=>clk);
  d6: fpd PORT MAP(d=> Q5, q=>Q6, clk=>clk);
  d7: fpd PORT MAP(d=> Q6, q=>Q7, clk=>clk);
  d8: fpd PORT MAP(d=> Q7, q=>Q8, clk=>clk);
  d9: fpd PORT MAP(d=> Q8, q=>Q9, clk=>clk);
```

```

d10: fpd PORT MAP(d=> Q9, q=>Q10, clk=>clk);
d11: fpd PORT MAP(d=> Q10, q=>Q11, clk=>clk);
d12: fpd PORT MAP(d=> Q11, q=>Q12, clk=>clk);
d13: fpd PORT MAP(d=> Q12, q=>Q13, clk=>clk);
d14: fpd PORT MAP(d=> Q13, q=>Q14, clk=>clk);
d15: fpd PORT MAP(d=> Q14, q=>Q15, clk=>clk);

```

```

led<= Q15&Q14&Q13&Q12&Q11&Q10&Q9&Q8&Q7&Q6&Q5&Q4&Q3&Q2&Q1&Q0;

```

```

end Behavioral;

```

shift_vector.vhd : Ping pong avec rebond sur bords de table et raquettes (=switchs)

```

entity shift_vector is

```

```

    Port ( btnC, btnU, btnL, btnR, btnD : in STD_LOGIC;
          sw : in STD_LOGIC_VECTOR (15 downto 0);
          led : out STD_LOGIC_VECTOR (15 downto 0);
          clk : in STD_LOGIC);

```

```

end shift_vector;

```

```

architecture Behavioral of shift_vector is

```

```

begin

```

```

    process(clk, sw)

```

```

        variable temp : STD_LOGIC_VECTOR (15 downto 0) := "0000000000000001";
        variable sens : STD_LOGIC := '0'; --'0' signifie de droite à gauche
        variable i : integer := 0;

```

```

    begin

```

```

        if (clk'event and clk='1') then

```

```

            if (sw(i)='1' or (temp(0)='1' and sens='1') or (temp(15)='1' and sens='0')) then

```

```

                sens := not sens;

```

```

            end if;

```

```

            if (sens='0') then

```

```

                temp := temp(14 downto 0) & temp(15);

```

```

                i := i+1;

```

```

            else

```

```

                temp := temp(0) & temp(15 downto 1);

```

```

                i := i-1;

```

```

            end if;

```

```

        end if;

```

```

        led <= temp;

```

```

    end process;

```

```

end Behavioral;

```

clk_div.vhd

```

entity clk_div is

```

```

    Port ( clk : in STD_LOGIC;
          clk_4hz : inout STD_LOGIC := '0');

```

```

end clk_div;

```


architecture Behavioral of clk_div is

```
begin
  process(clk)
    variable counter : unsigned(23 downto 0):= (others => '0');
  begin
    if (clk'event and clk='1') then
      counter := counter+1;
      if(counter=X"BEBC20") then
        counter := (others => '0');
        clk_4hz <= NOT clk_4hz;
      end if;
    end if;
  end process;
end Behavioral;
```

chenillard.vhd

entity chenillard is

```
  Port ( btnC, btnU, btnL, btnR, btnD : in STD_LOGIC;
        sw : in STD_LOGIC_VECTOR (15 downto 0);
        led : out STD_LOGIC_VECTOR (15 downto 0);
        clk : in STD_LOGIC);
```

end chenillard;

architecture Behavioral of chenillard is

```
signal new_clk : std_logic;
```

component clk_div

```
  Port ( clk : in STD_LOGIC;
        clk_4hz : inout STD_LOGIC := '0');
```

end component;

component shift_vector

```
  Port ( btnC, btnU, btnL, btnR, btnD : in STD_LOGIC;
        sw : in STD_LOGIC_VECTOR (15 downto 0);
        led : out STD_LOGIC_VECTOR (15 downto 0);
        clk : in STD_LOGIC);
```

end component;

begin

```
  clock : clk_div PORT MAP(clk=> clk, clk_4hz=>new_clk);
  shift_v : shift_vector PORT MAP(btnC=>btnC, btnU=>btnU, btnL=>btnL, btnR=>btnR,
                                  btnD=>btnD, sw=>sw, led=>led, clk=>new_clk);
```

end Behavioral;

btn_to_number.vhd

```
entity btn_to_number is
  Port ( btnR : in STD_LOGIC;
        btnD : in STD_LOGIC;
        btnL : in STD_LOGIC;
        btnU : in STD_LOGIC;
        num : out STD_LOGIC_VECTOR (1 downto 0);
        isP : OUT STD_LOGIC);
end btn_to_number;

architecture Behavioral of btn_to_number is

  signal s : STD_LOGIC_VECTOR(2 downto 0);
  signal btn : STD_LOGIC_VECTOR(3 downto 0);

begin
  btn <= btnR & btnD & btnL & btnU;
  s <= "100" when (btn = "1000") else
    "101" when (btn = "0100") else
    "110" when (btn = "0010") else
    "111" when (btn = "0001") else
    "000";
  num <= s(1 downto 0);
  isP <= s(2);
end Behavioral;
```

btn_pulse.vhd

```
entity btn_pulse is
  Port ( inp : in STD_LOGIC;
        E : in STD_LOGIC;
        clk : in STD_LOGIC;
        outp : out STD_LOGIC);
end btn_pulse;

architecture Behavioral of btn_pulse is

  signal q0, q1, q2, q3, q4, q5, o1 : std_logic;

begin
  process (clk)
  begin
    if (clk'event and clk = '1') then
      if E = '1' then
        q0 <= inp;
        q1 <= q0;
        q2 <= q1;
      end if;
      q3 <= o1;
      q4 <= q3;
      q5 <= q4;
    end if;
  end process;
end process;
```

```

o1 <= q0 and q1 and q2;
outp <= q3 and q4 and not(q5) ;
end Behavioral;

```

clkdiv.vhd (= Enable190 = clk190) => E190 qui produit une impulsion durant 10ns à la fréquence de 190Hz. Le clk190 est une clock de fréquence 190Hz.

```

entity clkdiv is
  Port ( clk : in  STD_LOGIC;
        reset : in  STD_LOGIC;
        E190, clk190 : out  STD_LOGIC);
end clkdiv;

architecture Behavioral of clkdiv is
  signal clkin: std_logic := '0';
begin
  process(clk,reset)
    variable q: std_logic_vector(23 downto 0):= X"0000000";
  begin
    if reset = '1' then
      q := X"0000000";
      clkin <= '0';
    elsif clk'event and clk = '1' then
      q := q+1;
      if Q(18)='1' and clkin='0' then
        E190 <= '1' ;
      else
        E190 <= '0';
      end if;
    end if;
    clkin<= Q(18);
  end process;

  clk190 <= clkin;
end Behavioral;

```

digicode.vhd

```

entity digicode is
  Port (clk : IN STD_LOGIC;
        sw : IN STD_LOGIC_VECTOR(7 downto 0);
        btnR, btnD, btnL, btnU, btnC : IN STD_LOGIC;
        led : OUT STD_LOGIC_VECTOR(1 downto 0));
end digicode;

architecture Behavioral of digicode is

  signal E190, clockdiv : STD_LOGIC;
  signal outBtnR, outBtnD, outBtnL, outBtnU, outBtnC : STD_LOGIC;

```

```

component btn_pulse
  Port ( inp : in STD_LOGIC;
        E : in STD_LOGIC;
        clk : in STD_LOGIC;
        outp : out STD_LOGIC);
end component;

component clkdiv
  Port ( clk : in STD_LOGIC;
        reset : in STD_LOGIC;
        E190, clk190 : out STD_LOGIC);
end component;

component fsm
  Port (clk : IN STD_LOGIC;
        sw : IN STD_LOGIC_VECTOR(7 downto 0);
        btnR, btnD, btnL, btnU, btnC : IN STD_LOGIC;
        led : OUT STD_LOGIC_VECTOR(1 downto 0));
end component;

begin
  cmp_clock : clkdiv port map (clk => clk, reset => '0', E190 => E190, clk190 => clockdiv);
  cmp_btnR : btn_pulse port map (inp => btnR, E => E190, clk => clockdiv, outp => outBtnR);
  cmp_btnD : btn_pulse port map (inp => btnD, E => E190, clk => clockdiv, outp => outBtnD);
  cmp_btnL : btn_pulse port map (inp => btnL, E => E190, clk => clockdiv, outp => outBtnL);
  cmp_btnU : btn_pulse port map (inp => btnU, E => E190, clk => clockdiv, outp => outBtnU);
  cmp_btnC : btn_pulse port map (inp => btnC, E => E190, clk => clockdiv, outp => outBtnC);
  cmp_fsm : fsm port map (clk => clockdiv, sw => sw, btnR => outBtnR, btnD => outBtnD, btnL =>
                        outBtnL, btnU => outBtnU, btnC => outBtnC, led => led);
end Behavioral;

```

digicode_chenillard.vhd

```

entity digicode_chenillard is
  Port (clk : IN STD_LOGIC;
        sw : IN STD_LOGIC_VECTOR(7 downto 0);
        btnR, btnD, btnL, btnU, btnC : IN STD_LOGIC;
        led : OUT STD_LOGIC_VECTOR(7 downto 0));
end digicode_chenillard;

```

architecture Behavioral of digicode_chenillard is

```

signal led_s : STD_LOGIC_VECTOR(1 downto 0);
signal led_chenillard_s : STD_LOGIC_VECTOR(15 downto 0);
signal clock_4Hz : STD_LOGIC;
signal reset: std_logic := '1';
signal count: integer := 0;

```

component digicode

```
Port (clk : IN STD_LOGIC;  
      sw : IN STD_LOGIC_VECTOR(7 downto 0);  
      btnR, btnD, btnL, btnU, btnC : IN STD_LOGIC;  
      led : OUT STD_LOGIC_VECTOR(1 downto 0));
```

end component;

component chenillard

```
Port ( btnC, btnU, btnL, btnR, btnD : in STD_LOGIC;  
      sw : in STD_LOGIC_VECTOR (15 downto 0);  
      led : out STD_LOGIC_VECTOR (15 downto 0);  
      clk : in STD_LOGIC);
```

end component;

component clk_div

```
Port ( clk : in STD_LOGIC;  
      clk_4hz : inout STD_LOGIC := '0');
```

end component;

begin

```
cmp_digicode : digicode port map (clk => clk, sw => sw, btnR => btnR, btnD => btnD, btnL =>  
btnL, btnU => btnU, btnC => btnC, led => led_s);
```

```
cmp_chenillard : chenillard port map (btnR => btnR, btnD => btnD, btnL => btnL, btnU => btnU,  
btnC => btnC, sw => "0000000010000000", led => led_chenillard_s, clk => clk);
```

```
cmp_clock : clk_div PORT MAP(clk => clk, clk_4hz => clock_4Hz);
```

```
process(clock_4Hz, led_s, btnC)
```

```
begin
```

```
if (btnC = '1') then
```

```
    reset <= '1';
```

```
    count <= 0;
```

```
end if;
```

```
if(clock_4hz'event and clock_4hz = '1') then
```

```
    if(led_s = "10" and reset='1') then
```

```
        led <= led_chenillard_s(7 downto 0);
```

```
        count <= count+1;
```

```
    elsif (led_s/="10" and reset='1') then
```

```
        led <= "000000"&led_s;
```

```
    end if;
```

```
    if (count = 8) then
```

```
        reset <= '0';
```

```
        count <= 0;
```

```
        led<= "00000000";
```

```
    end if;
```

```
end if;
```

```
end process;
```

end Behavioral;

fsm.vhd

entity fsm is

```
Port (clk : IN STD_LOGIC;  
      sw : IN STD_LOGIC_VECTOR(7 downto 0);  
      btnR, btnD, btnL, btnU, btnC : IN STD_LOGIC;  
      led : OUT STD_LOGIC_VECTOR(1 downto 0));
```

end fsm;

architecture Behavioral of fsm is

```
type state_type is (s1, s2, s3, s4, sOpen);  
signal state, next_state : state_type;  
signal sig_i : std_logic_vector(1 downto 0);  
signal btn : STD_LOGIC_VECTOR(1 downto 0);  
signal btnP : STD_LOGIC;
```

component btn_to_number

```
Port ( btnR : in STD_LOGIC;  
       btnD : in STD_LOGIC;  
       btnL : in STD_LOGIC;  
       btnU : in STD_LOGIC;  
       num : out STD_LOGIC_VECTOR (1 downto 0);  
       isP : OUT STD_LOGIC);
```

end component;

begin

SYNC_PROC : process (clk, btnC)

begin

if rising_edge(clk) then

if (btnC = '1') then

state <= s1;

led <= "00";

else

state <= next_state;

led <= sig_i;

end if;

end if;

end process;

OUTPUT_DECODE : process (state)

begin

case (state) is

when sOpen =>

sig_i <= "10";

when s1 =>

sig_i <= "00";

when others =>

sig_i <= "01";

end case;

end process;

```
cmp : btn_to_number port map (btnR => btnR, btnD => btnD, btnL => btnL, btnU => btnU, num =>
btn, isP=>btnP);
```

```
NEXT_STATE_DECODE : process (state, sw, btnP, btn)
```

```
begin
```

```
    next_state <= state;
```

```
    if (btnP='1') then
```

```
        case (state) is
```

```
            when s1 =>
```

```
                if (sw(1 downto 0)=btn) then
```

```
                    next_state <= s2;
```

```
                else
```

```
                    next_state <= s1;
```

```
                end if;
```

```
            when s2 =>
```

```
                if (sw(3 downto 2)=btn) then
```

```
                    next_state <= s3;
```

```
                else
```

```
                    next_state <= s1;
```

```
                end if;
```

```
            when s3 =>
```

```
                if (sw(5 downto 4)=btn) then
```

```
                    next_state <= s4;
```

```
                else
```

```
                    next_state <= s1;
```

```
                end if;
```

```
            when s4 =>
```

```
                if (sw(7 downto 6)=btn) then
```

```
                    next_state <= sOpen;
```

```
                else
```

```
                    next_state <= s1;
```

```
                end if;
```

```
            when others =>
```

```
                next_state <= state;
```

```
        end case;
```

```
    end if;
```

```
end process;
```

```
end Behavioral;
```

afficheur_16bits.vhd

entity afficher_16bits is

```
Port (clk : IN STD_LOGIC;  
      sw : IN STD_LOGIC_VECTOR (15 downto 0);  
      seg : OUT STD_LOGIC_VECTOR (6 downto 0);  
      an : OUT STD_LOGIC_VECTOR (3 downto 0));
```

end afficher_16bits;

architecture Behavioral of afficher_16bits is

```
signal clockdiv : STD_LOGIC;  
signal an_s : STD_LOGIC_VECTOR (3 downto 0);  
signal sw_7seg : STD_LOGIC_VECTOR (3 downto 0);
```

component x7seg

```
Port ( sw : in STD_LOGIC_VECTOR (3 downto 0);  
      sevenseg : out STD_LOGIC_VECTOR (6 downto 0));
```

end component;

component clk190

```
Port ( clk : in STD_LOGIC;  
      reset : in STD_LOGIC;  
      E190, clk190 : out STD_LOGIC);
```

end component;

component fsm_seg

```
Port (clk : IN STD_LOGIC;  
      an : OUT STD_LOGIC_VECTOR (3 downto 0));
```

end component;

begin

```
cmp_clock : clk190 port map (clk => clk, reset => '0', E190 => open, clk190 => clockdiv);  
cmp_7seg : x7seg port map (sw => sw_7seg, sevenseg => seg);  
cmp_fsm : fsm_seg port map (clk => clockdiv, an => an_s);
```

with an_s select

```
sw_7seg <= sw(3 downto 0) when "1110",  
          sw(7 downto 4) when "1101",  
          sw(11 downto 8) when "1011",  
          sw(15 downto 12) when others;
```

```
an <= an_s;
```

end Behavioral;

fsm_seg.vhd

```
entity fsm_seg is
  Port (clk : IN STD_LOGIC;
        an : OUT STD_LOGIC_VECTOR (3 downto 0));
end fsm_seg;
```

architecture Behavioral of fsm_seg is

```
type state_type is (st1, st2, st3, st4);
signal anodes_s : STD_LOGIC_VECTOR (3 downto 0);
signal state, next_state : state_type;
```

```
begin
```

```
  SYNC_PROC : process (clk)
```

```
  begin
```

```
    if rising_edge(clk) then
```

```
      state <= next_state;
```

```
      an <= anodes_s;
```

```
    end if;
```

```
  end process;
```

```
  OUTPUT_DECODE: process (state)
```

```
  begin
```

```
    if (state = st1) then
```

```
      anodes_s <= "1110";
```

```
    elsif (state = st2) then
```

```
      anodes_s <= "1101";
```

```
    elsif (state = st3) then
```

```
      anodes_s <= "1011";
```

```
    else
```

```
      anodes_s <= "0111";
```

```
    end if;
```

```
  end process;
```

```
  NEXT_STATE_DECODE: process (state)
```

```
  begin
```

```
    next_state <= state;
```

```
    case (state) is
```

```
      when st1 =>
```

```
        next_state <= st2;
```

```
      when st2 =>
```

```
        next_state <= st3;
```

```
      when st3 =>
```

```
        next_state <= st4;
```

```
      when st4 =>
```

```
        next_state <= st1;
```


```
      when others =>
```

```
        next_state <= st1;
```

```
    end case;
```

```
  end process;
```

```
end Behavioral;
```

 

add.hmd (additionneur mots de 16 bits non signé, résultats sur 17 bits => 16 bits de poids faibles, et en allumant la LED0 en cas de retenue)

```
0c00 0000 0014 ffff
201f a402 8804 201f
a402 8804 c820 8002
2010 c82b a003 03f5
1400 ffff ffff ffff
1000 0000 0004 1c00
ffff ffff ffff ffff
1c00 ffff ffff ffff
ffff ffff ffff ffff
```

random.vhd

```
entity random is
  generic ( width : integer := 32 );
  port (
    clk , reset : in std_logic;
    enable : in std_logic;
    random_num : out std_logic_vector (width-1 downto 0) --output vector
  );
end random;
```

architecture Behavioral of random is

```
  signal r : std_logic_vector(31 downto 0) := x"80000000";
```

```
begin
  process(clk)
  begin
    if ( clk'event and clk = '1' ) then
      if (reset = '1') then
        r <= x"80000000";
      elsif(enable = '1') then
        r(30 downto 0) <= r(31 downto 1);
        r(31) <= (((r(0) xor r(2)) xor r(3)) xor r(4));
      end if;
      random_num <= r;
    end if;
  end process;
end Behavioral;
```

IP_rdm.vhd

entity IP_rdm is

 GENERIC (Mycode : std_logic_vector(10 downto 0) := "00000010000"

);

 port (

 clk , reset : in std_logic;

 IPcode : in std_logic_vector (10 downto 0);

 Tout : out std_logic_vector (31 downto 0);

 Nout : out std_logic_vector (31 downto 0)

);

end IP_rdm;

architecture Behavioral of IP_Rdm is

 component random

 generic (width : integer := 32);

 port (

 clk , reset : in std_logic;

 enable : in std_logic;

 random_num : out std_logic_vector (width-1 downto 0) --output vector

);

 end component;

 signal enable_s : STD_LOGIC;

 signal random_num_s : std_logic_vector (31 downto 0);

begin

 cmp : random port map (clk => clk, reset => reset, enable => enable_s, random_num =>
 random_num_s);

 enable_s <= '1' when ipcode(10 downto 0)= Mycode else '0';

 -- Tout <= random_num_s when ipcode(10 downto 0)= Mycode else (others =>'Z');

 Tout <= "0000000000000000000000" & random_num_s(11 downto 0) when ipcode(10 downto
 0)= Mycode else (others =>'Z');

 Nout <= "0000000000000000000000" & random_num_s(23 downto 12) when ipcode(10 downto
 0)= Mycode else (others =>'Z');

end Behavioral;

IP_square2.vhd

```
entity IP_square2 is
  GENERIC (Mycode : std_logic_vector(10 downto 0):="000000000000" );
  Port ( Tin : in  STD_LOGIC_VECTOR (31 downto 0);
        Nin : in  STD_LOGIC_VECTOR (31 downto 0);
        IPcode : in  STD_LOGIC_vector(10 downto 0) ;
        Tout : out STD_LOGIC_VECTOR (31 downto 0));
end IP_square2;

architecture Behavioral of IP_square2 is
  component multiply
    port (
      a: in std_logic_vector(15 downto 0);
      b: in std_logic_vector(15 downto 0);
      p: out std_logic_vector(31 downto 0));
  end component;

  signal mul1, mul2 : STD_LOGIC_VECTOR (31 downto 0);

begin
  my_mul16_1 : multiply port map (a => Tin(15 downto 0), b => Tin (15 downto 0), p => mul1);
  my_mul16_2 : multiply port map (a => Nin(15 downto 0), b => Nin (15 downto 0), p => mul2);
  Tout <= (mul1+mul2) when Mycode = IPcode else (others =>'Z');
end Behavioral;
```

IP_cmpFFE001.vhd

```
entity IP_cmpFFE001 is
  GENERIC (Mycode : std_logic_vector(10 downto 0) := "000000000000");
  port ( Tin : in std_logic_vector (31 downto 0);
        IPcode : in std_logic_vector (10 downto 0);
        Tout : out std_logic_vector(31 downto 0));
end IP_cmpFFE001;

architecture Behavioral of IP_cmpFFE001 is

  signal s : std_logic_vector(31 downto 0);

begin
  process(Tin)
  begin
    if(Tin <= x"00FFE001") then
      s <= x"00000001";
    else
      s <= x"00000000";
    end if;
  end process;

  Tout <= s when IPcode = Mycode else (others =>'Z');
end Behavioral;
```

IP_detecte_fin.vhd

```
entity IP_detecte_fin is
  GENERIC (Mycode : std_logic_vector(10 downto 0) := "000000000000");
  port (
    Tin : in std_logic_vector (31 downto 0);
    IPcode : in std_logic_vector (10 downto 0);
    Tout : out std_logic_vector(31 downto 0)
  );
end IP_detecte_fin;
```

architecture Behavioral of IP_detecte_fin is

```
signal s : std_logic_vector(31 downto 0);
```

```
begin
  process(Tin)
  begin
    if(Tin <= 0) then
      s <= x"FFFFFFFF";
    else
      s <= x"00000000";
    end if;
  end process;
  Tout <= s when IPcode = Mycode else (others =>'Z');
end Behavioral;
```

IP_generateFFFF.vhd

```
entity IP_generate_FFFF is
  GENERIC (Mycode : std_logic_vector(10 downto 0) := "000000000000");
  port (
    IPcode : in std_logic_vector (10 downto 0);
    Tout : out std_logic_vector(31 downto 0)
  );
end IP_generate_FFFF;
```

architecture Behavioral of IP_generate_FFFF is

```
begin
  Tout <= x"00010001" when ipcode= Mycode else (others =>'Z');
end Behavioral;
```

<u>add32.fsh</u> lit 2 nbr de 16 bits, les place sur la pile et affiche le résultat sur l'afficheur 7seg pour les 16 bits de poids faibles et le 17ieme bit sur les led	<u>rdm.fsh</u> affiche les 16 bits de poids faibles du 50ième nombre aléatoire de la série en utilisant IP rdm	<u>pi.fsh</u> :IP rdm \$8810; slave start master : main ticraz 0 \$10000 for rdm dup \$fff and dup mul16 swap 12 -> \$fff and dup mul16 add \$ffe001 <= if inc endif next tic swap 7seg \$1f btn dup 16 -> 7seg \$1f btn 7seg \$1f btn ; start main endprogram	<u>pi f.fsh</u> :IP rdm \$9010; :IP square2 \$C814; :IP cmpFFE001 \$AB00; :IP detectefin \$AB01; :IP generateFFFF \$8B02; slave start master : main ticraz 0 generateFFFF begin swap rdm square2 cmpFFE001 add swap dec dup detectefin until pop tic swap 7seg \$1f btn dup 16 -> 7seg \$1f btn 7seg \$1f btn ; start main endprogram
slave start master :lire_switch \$1f btn switch ; : main lire_switch lire_switch + 7segdup \$10 -> led ; start main \$1f btn endprogram	:IP rdm \$8810; :IP rdm2 \$8010; slave start master : main \$30 for rdm2 next rdm 7seg ; start main \$1f btn endprogram		